



Design Solution 11

SP6682HV Boost from Li-ion input to 9 WLED output at 20mA

Date: Jan.10, 2006

Designed by: Brian Kennedy (bkennedy@sipex.com)

Part Number: SP6682EU

Application Description: Powering LED display backlight

Electrical Requirements:

Input Voltage	3.0V – 4.2V
Output Voltage	29V – 31V (9 White LEDs)
Output Current	20mA

Circuit Description:

This circuit has been designed to provide 29V to 31V output at 20mA for powering 9 White LEDs in series for LCD backlight applications. High output voltage and low cost dictated the choice of the controller and external components. In order to reduce cost, a non-synchronous boost regulator topology was chosen. The SP6682 is a charge pump regulator that is being used instead as a boost DC/DC controller to drive an N-channel MOSFET for charging the inductor in the discontinuous mode. As a non-synchronous boost, a second MOSFET driver is not needed and instead a small inexpensive MBR0540 Schottky diode is used in the discharge phase to charge the output capacitor. An output over-voltage protection circuit is an option provided by simply adding a Zener diode and resistor. High switching frequency (600 kHz) allows the use of a small 3.3uH inductor and two 1uF ceramic output capacitors.

This report includes the application schematic complete with component part numbers and figures 1-3 illustrating electrical performance of the design.

Design Solution 11

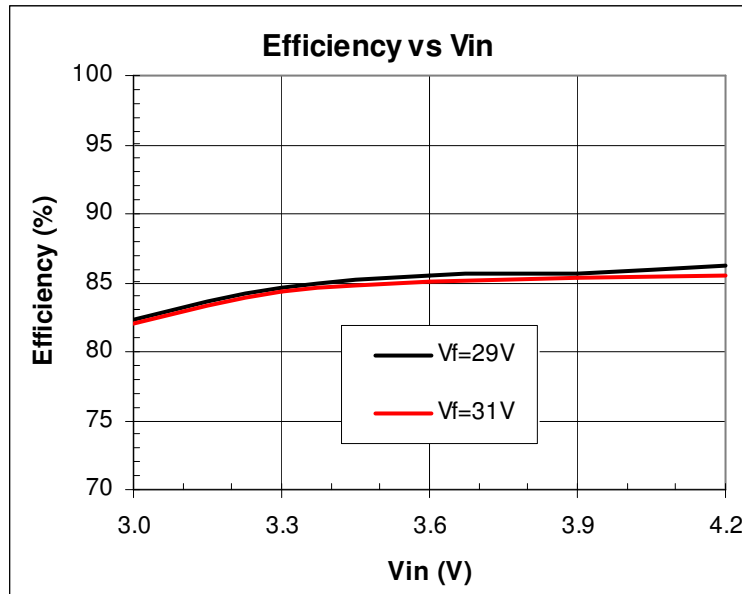


Figure 1. Efficiency Graph

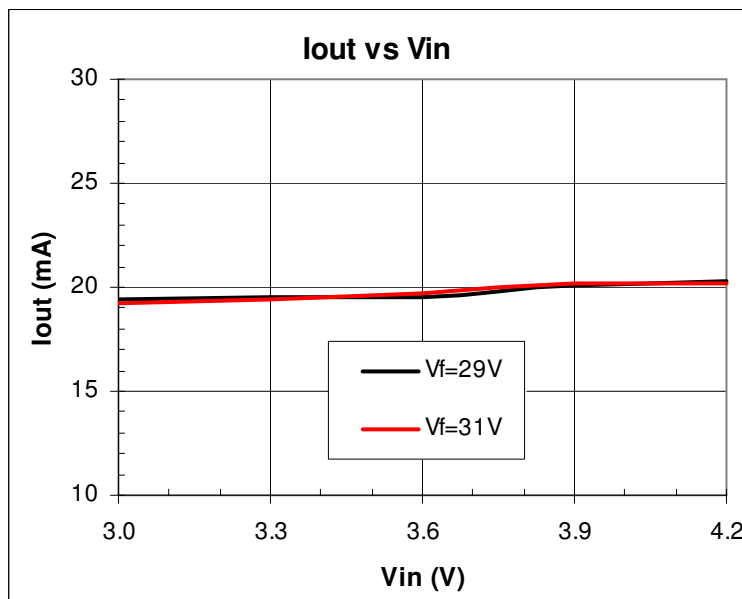


Figure 2. Output Current Graph

Design Solution 11

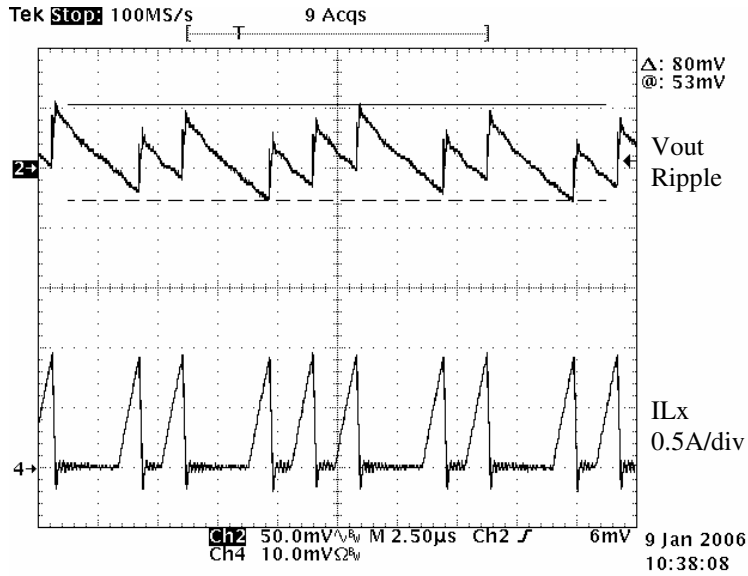


Figure 3. Output Noise and Inductor Current

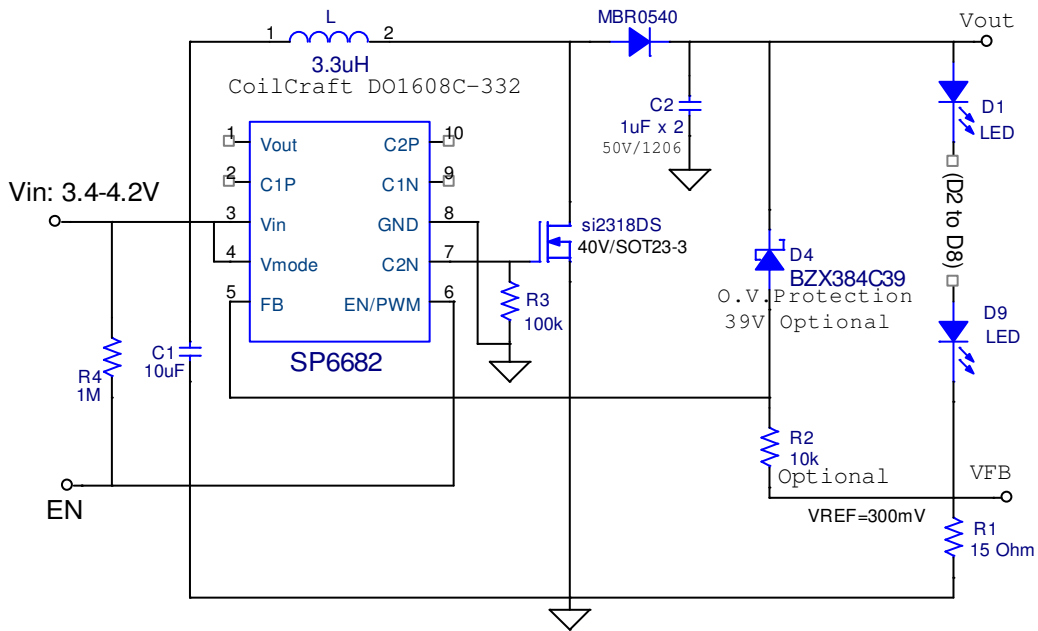


Figure 4. Application Schematic