

SP6648: 3.0V to 3.2V input to 4.7V output at 70mA

Part Number: SP6648ER


Application Description: 3.0V to 3.2V converted to 4.7V at 70mA output

Electrical Requirements:

Input Voltage	3.0V to 3.2V
Output Voltage	4.7V
Output Current	70mA

Circuit Description:

This application has been designed for a 4.7V output that requires up to 70mA output current in a small solution size with low output ripple. The SP6648 boost regulator uses pulse frequency mode control with a 20uA quiescent current to provide excellent light load efficiency. All the external components have been optimized for an output current up to 70mA output which includes a small 1210 size inductor and 0805 size 10uF capacitors. The circuit has been designed with 0.1ohm ESR resistor in series with the output and a small 220pF feed-forward capacitor to minimize output ripple. This report includes figure 7 application schematic complete with component part numbers and figures 1-6 illustrating electrical performance of the design.

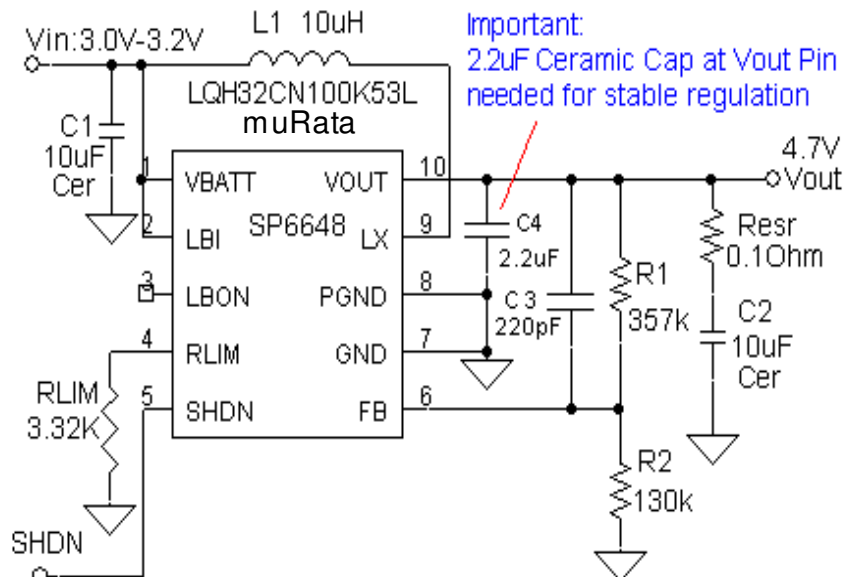

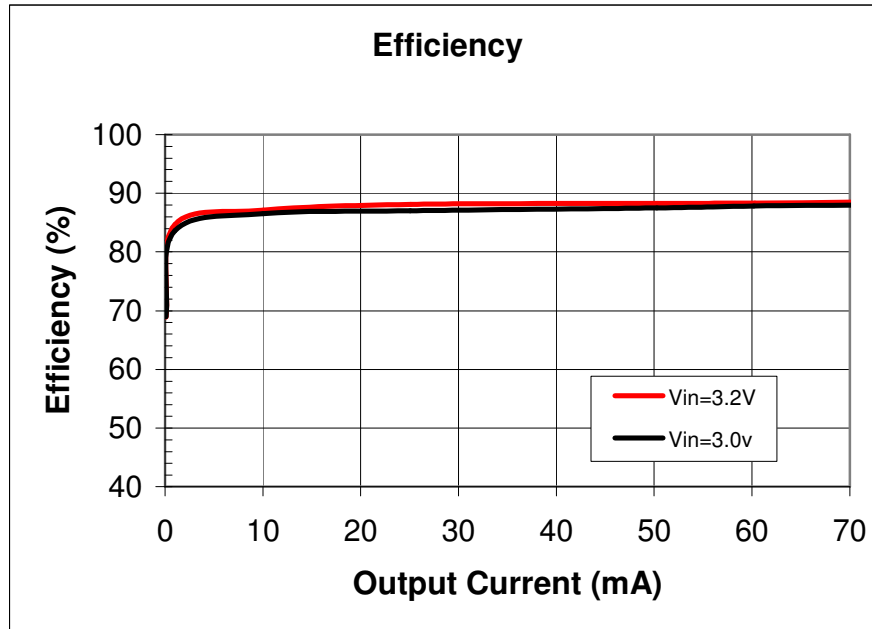


Figure 1. Efficiency Graph


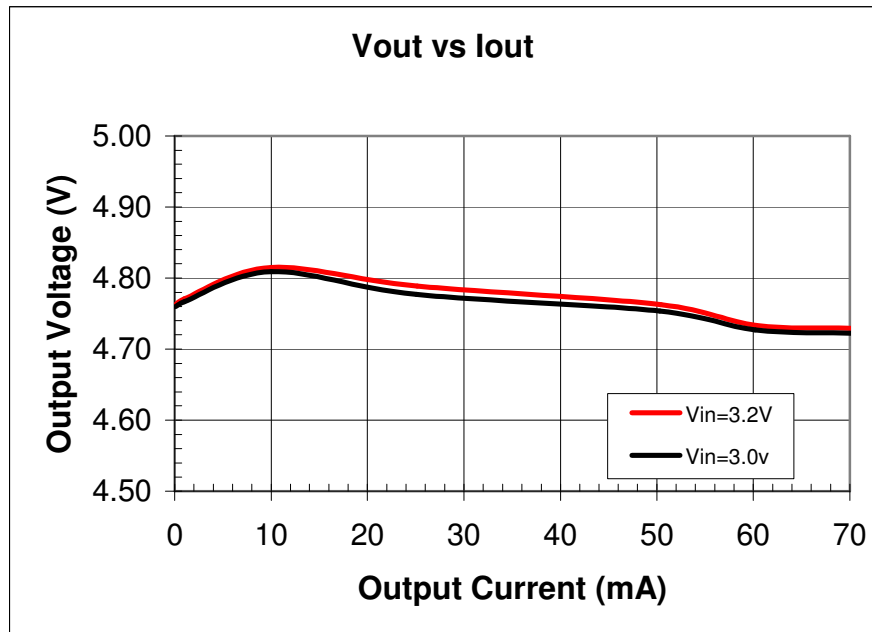


Figure 2. Vout Vs Iout

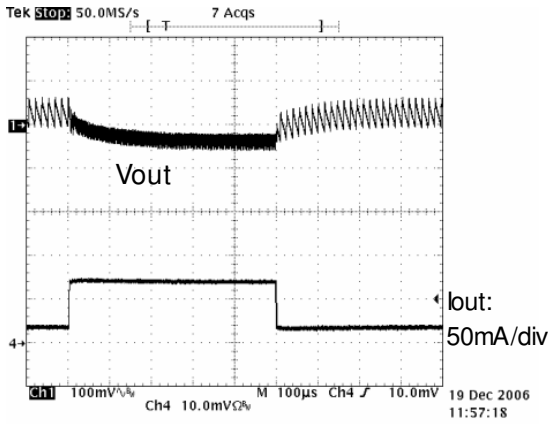

Vin=3.0V, Iout step = 20mA to 70mA

Figure 3. 3.0V Transient Response


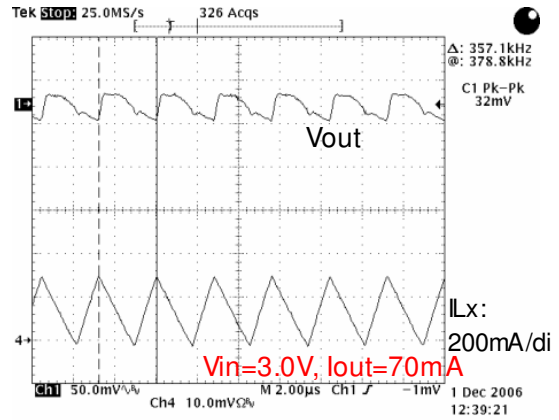


Figure 4. 3.0V Output Ripple

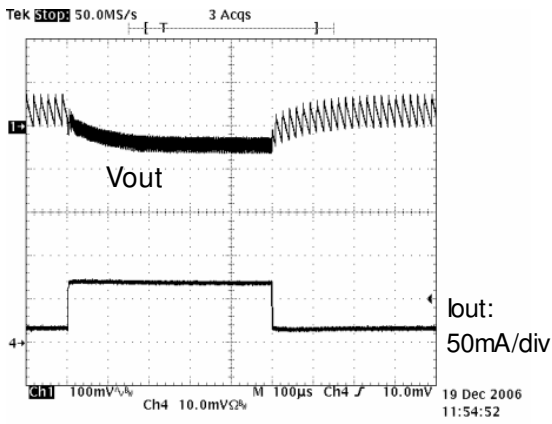

Vin=3.2V, Iout step = 20mA to 70mA

Figure 5. 3.2V Transient Response


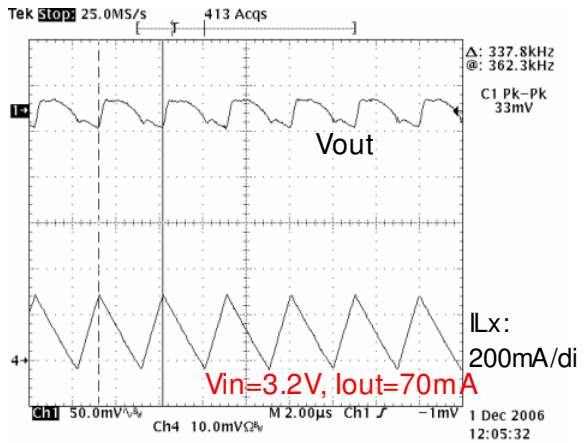


Figure 6. 3.2V Output Ripple

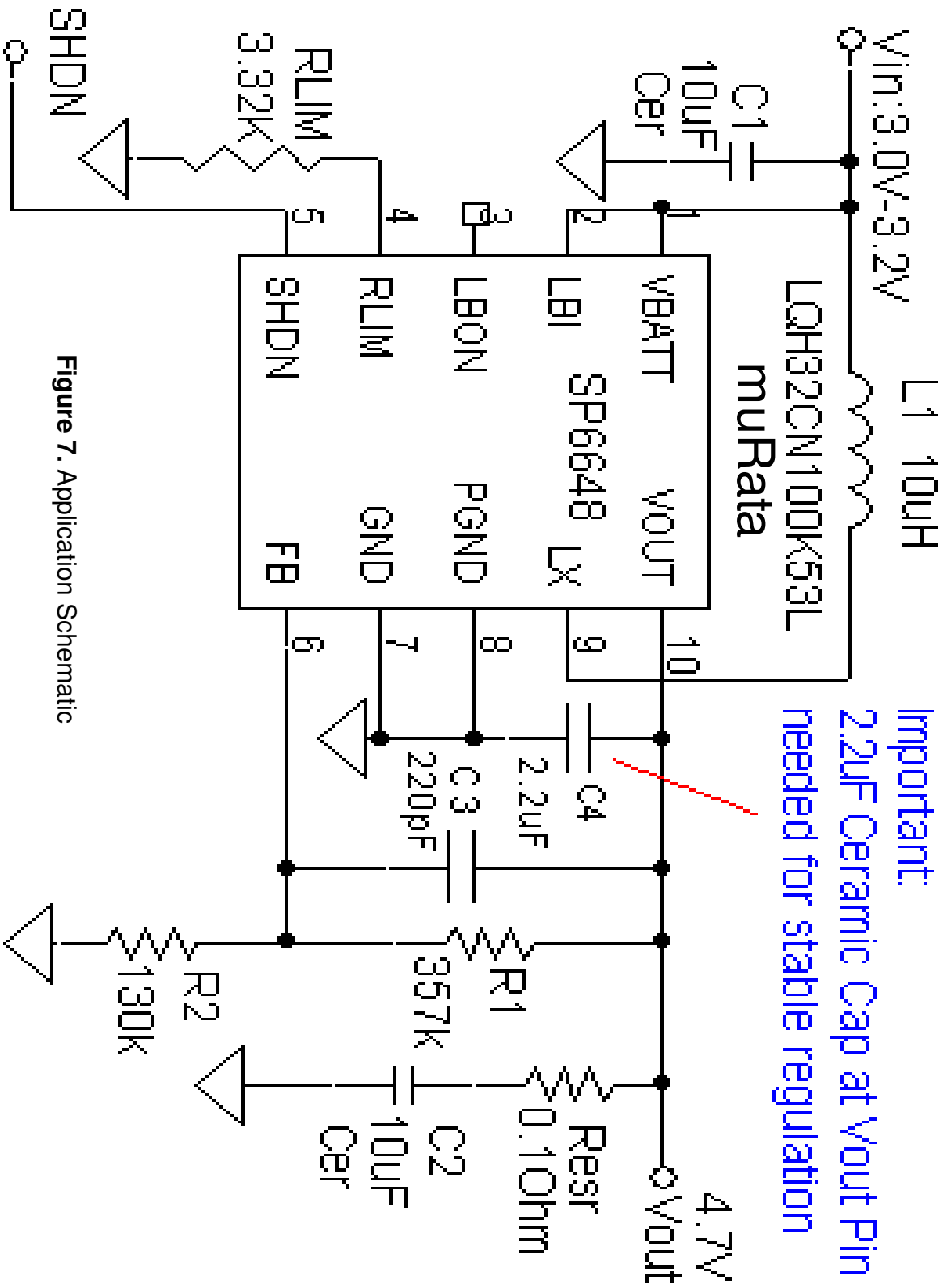

Important:
2.2uF Ceramic Cap at Vout Pin
needed for stable regulation

Figure 7. Application Schematic

For further assistance:

Email: Sipexsupport@sipex.com
WWW Support page: <http://www.sipex.com/content.aspx?p=support>
Live Technical Chat: <http://www.geolink-group.com/sipex/>
Sipex Application Notes: <http://www.sipex.com/applicationNotes.aspx>



Sipex Corporation

**Headquarters and
Sales Office**
233 South Hillview Drive
Milpitas, CA95035
tel: (408) 934-7500
faX: (408) 935-7600

Sipex Corporation reserves the right to make changes to any products described herein. Sipex does not assume any liability arising out of the application or use of any product or circuit described herein; neither does it convey any license under its patent rights nor the rights of others.