

## SP6136 Buck Regulator: 3.3V Input to 1.2V @ 0-10A Output

**Designed by:** Shahin Maloyan

**Part Number:** SP6136ER1

**Application Description:** Low-voltage Point-of-Load


**Electrical Requirements:**


Input Voltage	3.3V
Output Voltage	1.2V
Output Current	0-10A

**Circuit Description:**


This buck converter has been designed to provide 1.2V output at 10A for Point-of-Load applications. The SP6136 is a high performance buck regulator controller that provides all necessary functions required by a buck regulator: over-current protection, power-good output, adjustable UVLO and Enable input. High switching frequency (600kHz) minimizes solution cost and size.

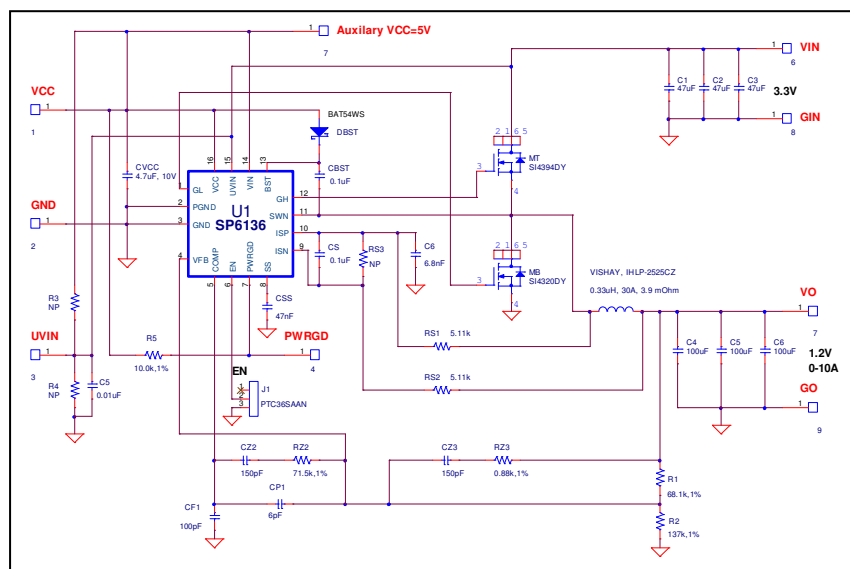This report includes the application schematic complete with component part numbers and figures 1-7 illustrating electrical performance of the design.




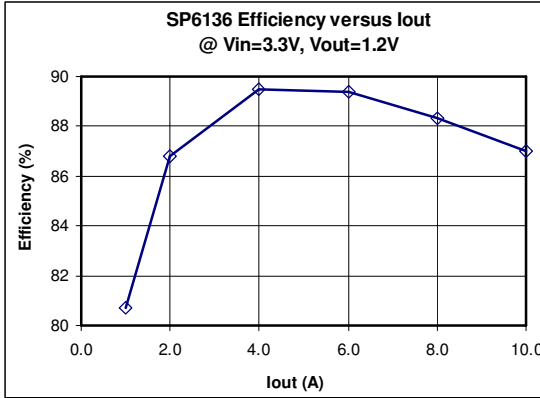


**Figure 1: Efficiency Graph**

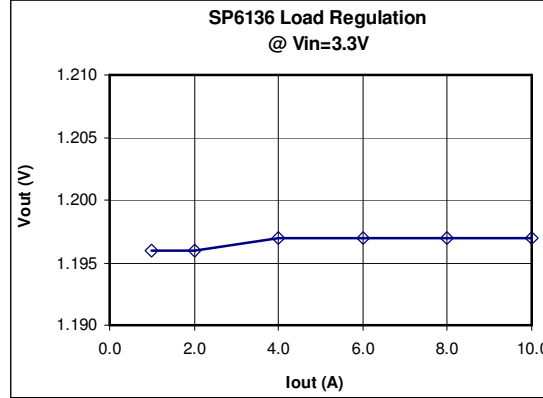


**Figure 2: VOUT Regulation Graph**

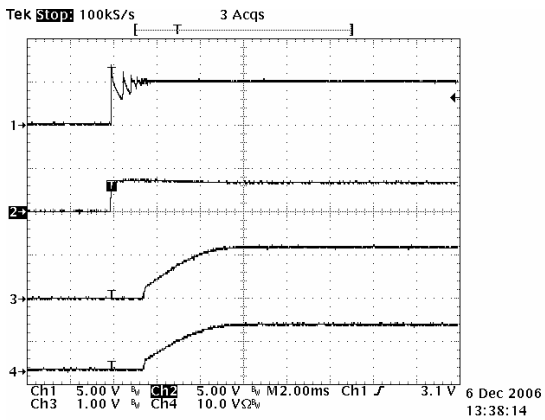


**Figure 3. Startup at  $I_o=10A$ , ch1:VCC, Ch2: Vin, ch3: Vout, ch4: Iout**

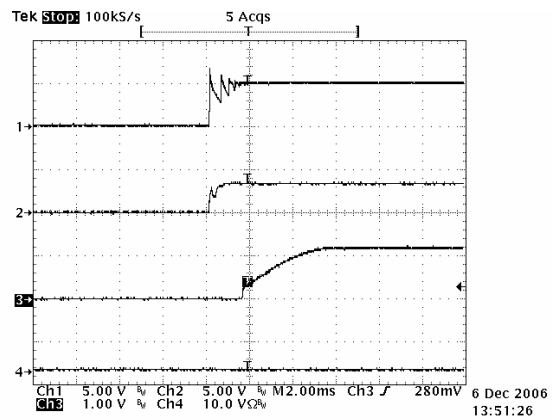


**Figure 4. Startup at  $I_o=0A$ , ch1:VCC, Ch2: Vin, ch3: Vout, ch4: Iout**

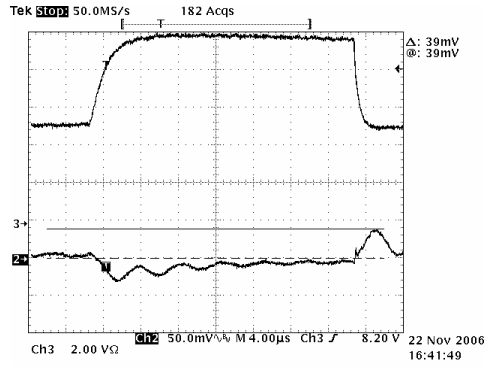


**Figure 5.** Step load response 5-10A

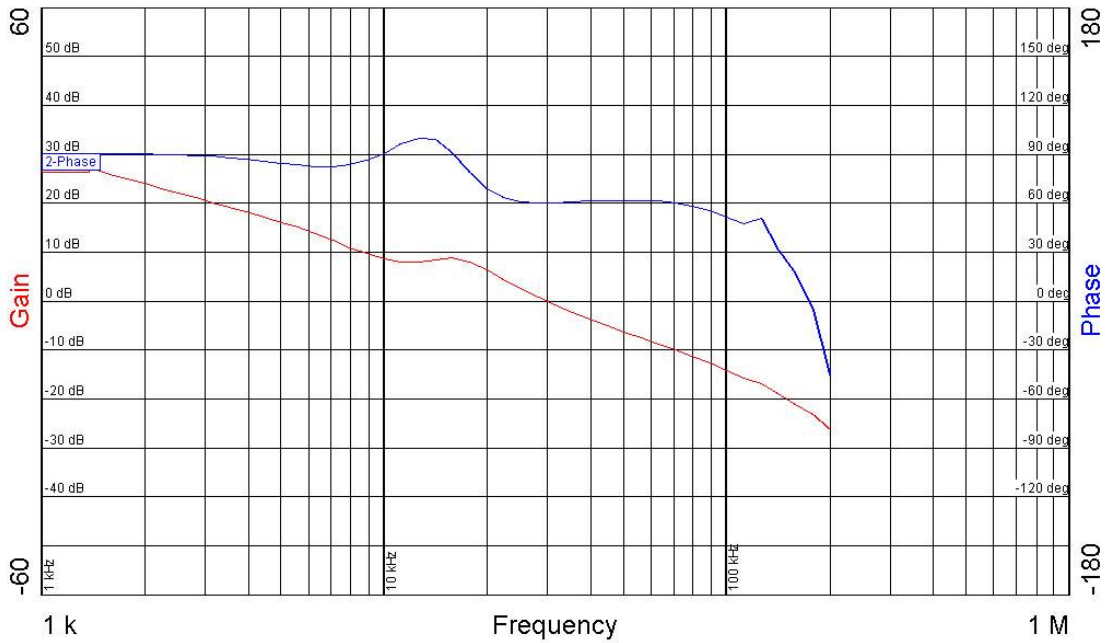

**Figure 6.** Loop gain-phase plot at  $I_o=10A$ ,  $f_c=30kHz$ , phase margin=60 degrees

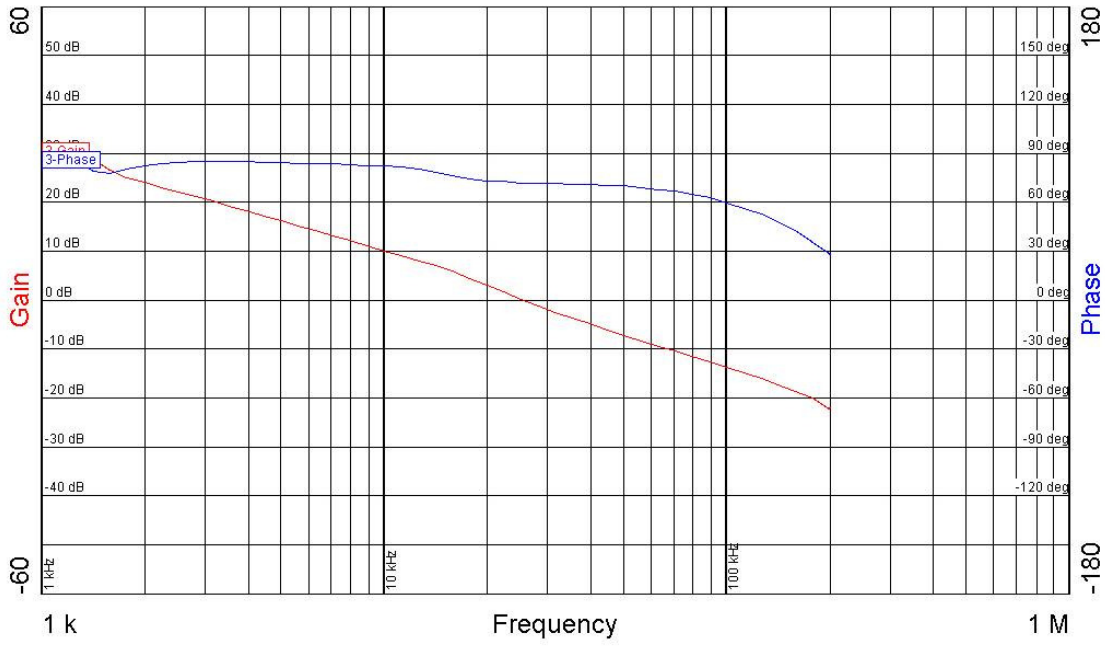

**Figure 7.** Loop gain-phase plot at  $I_o=0A$ ,  $f_c=25kHz$ , phase margin=70 degrees

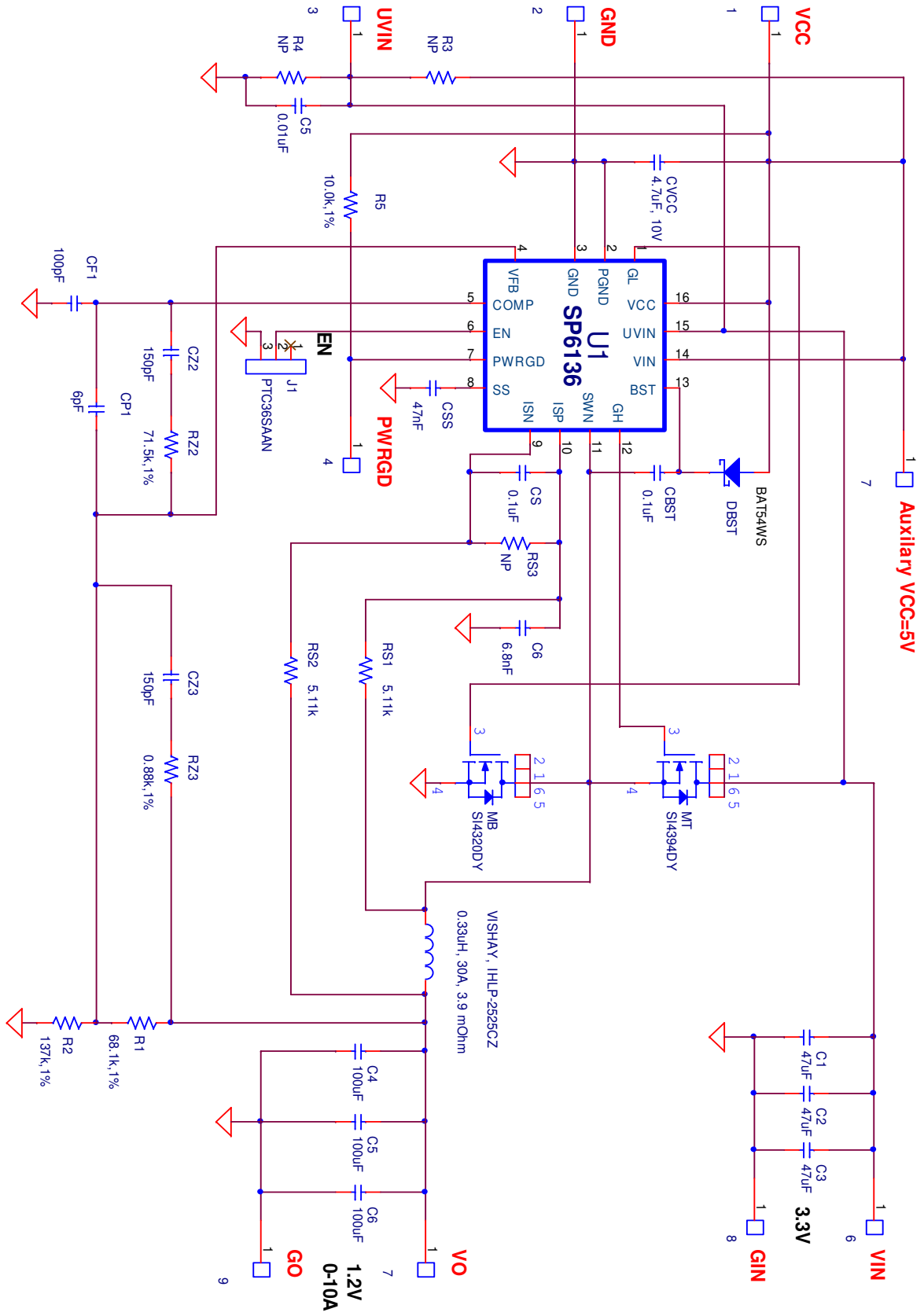

Circuit Schematic

For further assistance:

Email: [Sipexsupport@sipex.com](mailto:Sipexsupport@sipex.com)  
WWW Support page: <http://www.sipex.com/content.aspx?p=support>  
Live Technical Chat: <http://www.geolink-group.com/sipex/>  
Sipex Application Notes: <http://www.sipex.com/applicationNotes.aspx>



## **Sipex Corporation**

**Headquarters and  
Sales Office**  
233 South Hillview Drive  
Milpitas, CA95035  
tel: (408) 934-7500  
faX: (408) 935-7600

Sipex Corporation reserves the right to make changes to any products described herein. Sipex does not assume any liability arising out of the application or use of any product or circuit described herein; neither does it convey any license under its patent rights nor the rights of others.