

SP7663 : 12V Input, 5 Volts out at 4Amps

Designed by: Tim Sullivan

Part Number: SP7663

Application Description: A SP7663 PowerBlox™ device is used to create a 5volt output from a 12volt source

Electrical Requirements:


Input Voltage	12V nominal (9.6V – 22V capable with this design)
Output Voltage	5.0V
Output Current	4 Amps

Circuit Description:


This circuit has been designed to provide 5.0 Volts from a 12Volt nominal input supply. It uses the PowerBlox™ solution SP7663 and 19 parts (not including PCB and I/O pins) and uses approximately 2 square inches of board space. It is possible to maintain this small area usage due to the incorporation of the high and low side FETs and the PWM controller into one package.

The solution uses a Wurth 10x10x4mm, low resistance inductor which is a good balance of size and performance for this solution. Ceramic capacitors were used on the converter input and output and a Type III feedback configuration was implemented to provide excellent transient response.

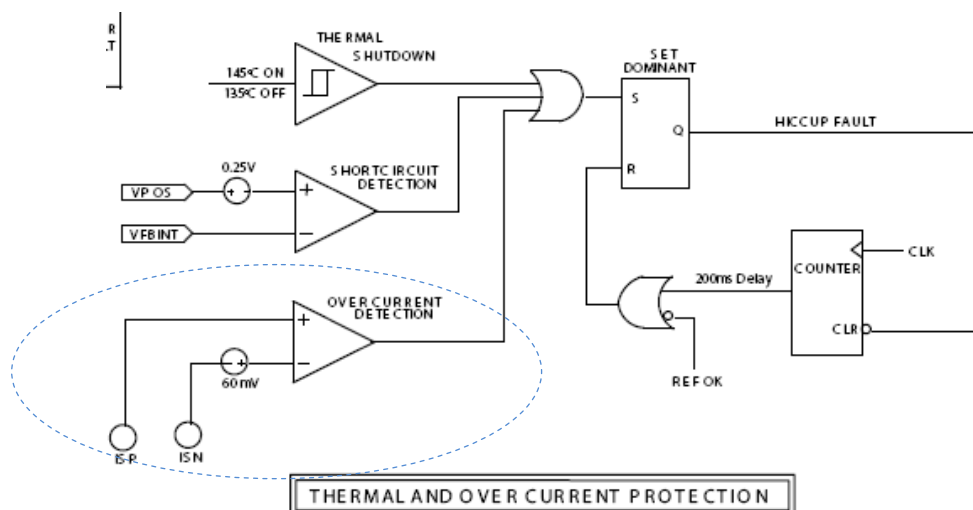
This example has been selected to illustrate the proper connection of the PowerBlox™ part with an output greater than 3.3Volts. Because of the limitations of the Overcurrent Detection internal comparator (controller schematic shown below), only voltages up to 3.3 volts can use the overcurrent protection feature. See the complete schematic in the report for a detailed schematic diagram.



Simplified Design Solution Schematic

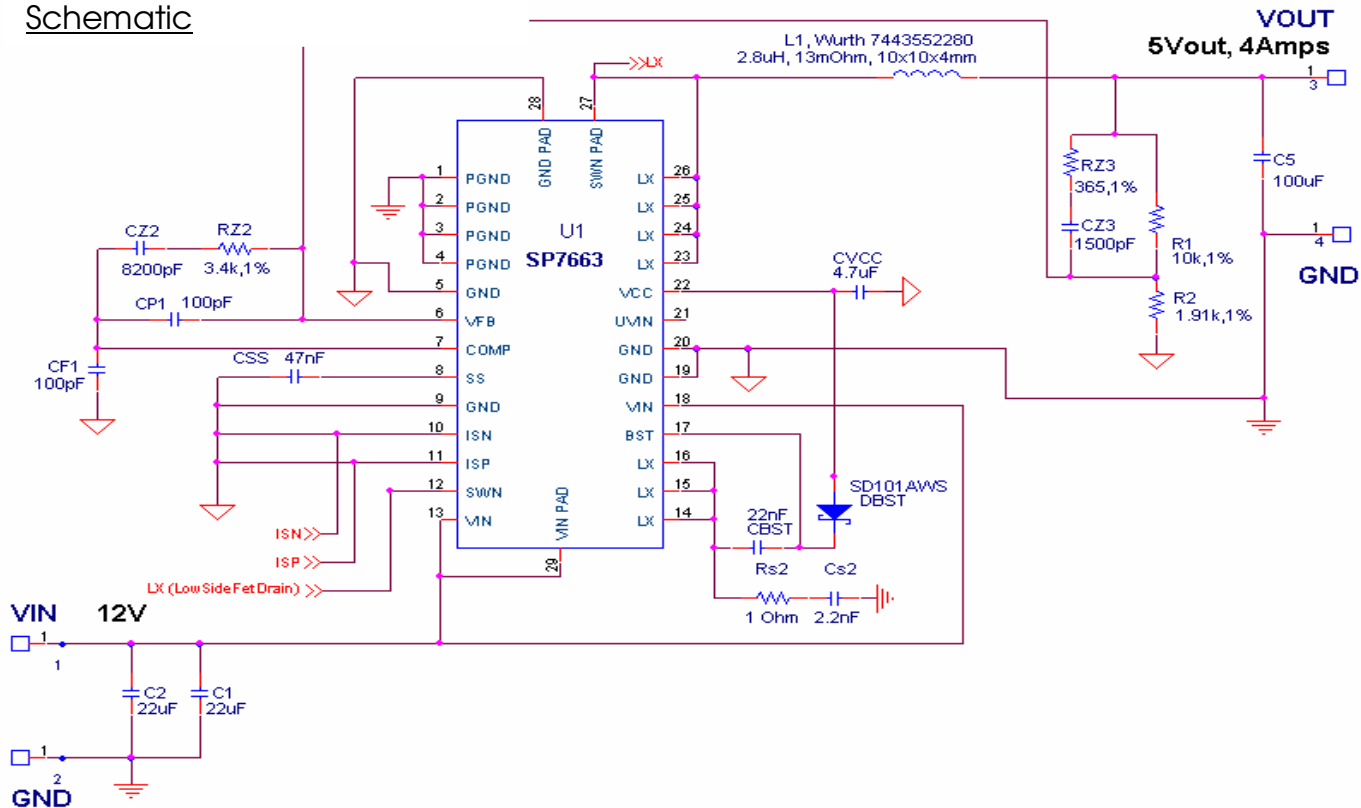


Note in the simplified version the components that are not used in the >3.3Vout design. Where 0Ω resistors were used, connections have been placed. By shorting ISN and ISP to ground the overcurrent circuitry in the controller is disabled. The converter will still have the short circuit protection feature. Note also the removal of R6, R7, C8, and R12. When a nominal 12Volts input is used, UVIN components are not required as the internal UVLO level is set to 9.6 volts.

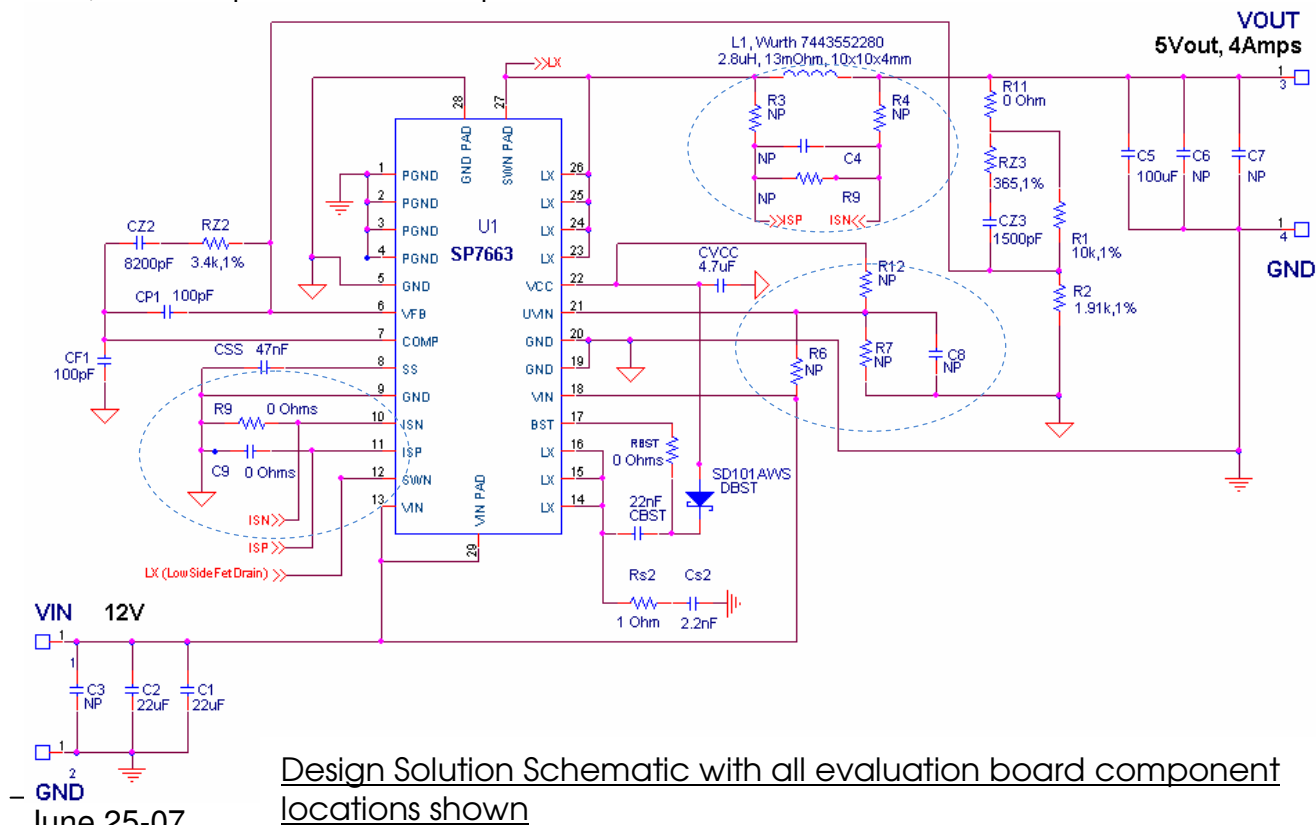


Design Solution Schematic with all evaluation board component locations shown

Efficiency and Load Regulation

7663 Efficiency
12Vin - 5Vout - 4Amp

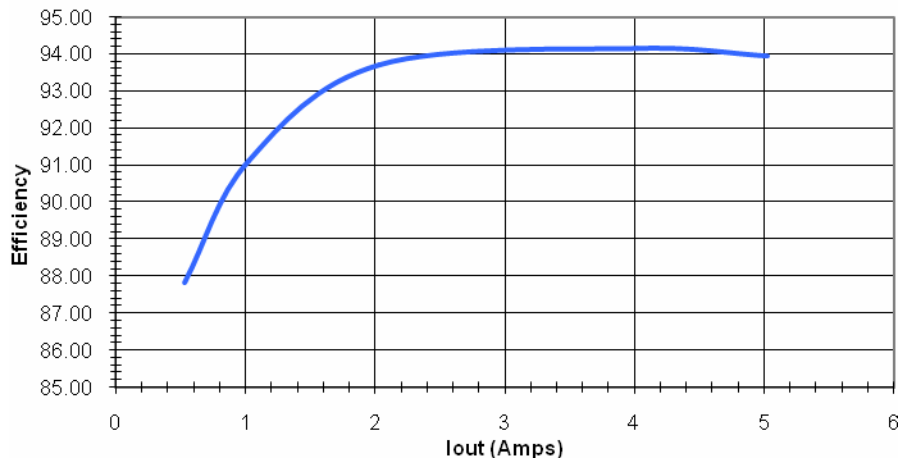

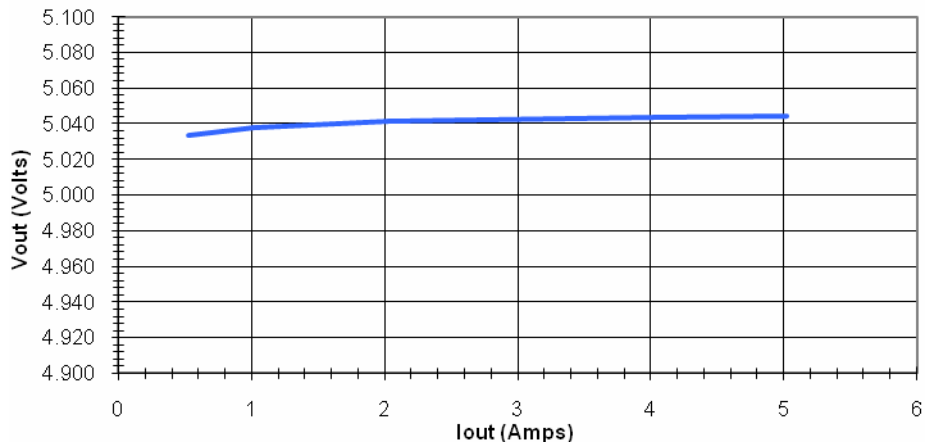7663 Load Regulation
12Vin - 5Vout - 4Amp




Performance Measurements

VIN	IIN(A)	VOUT	IOUT(A)	Efficiency	POUT (W)	PDISS(W)	PDISS PB(W)	Output Ripple
12.01	2.25	5.044	5.02	93.94	25.32	1.63	1.56	29mV
12.02	1.79	5.043	4.02	94.14	20.27	1.26	1.21	29mV
12.04	0.91	5.041	2.03	93.71	10.23	0.69	0.67	27mV
12.05	0.47	5.038	1.02	91.12	5.14	0.50	0.50	26mV
12.06	0.25	5.034	0.53	87.81	2.67	0.37	0.37	25mV

Load Regulation 0.204 %

Converter Bill of Materials:

SP7663		12Vin 5Vout				
Line No.	Ref. Des.	Qty.	Manufacturer	Layout Size	Component	Vendor Phone #
1	PCB	1	Sipex		SP7663EB	978-667-8700
2	U1	1	Sipex	DFN-26	7663 Buck Regulator	978-667-8700
3	DBST	1	Vishay Semi	SOD-323	SD101AWS 15mA-30V Schottky	800-344-4539
4	L1	1	Würth	10x10mm	2.8uH, 13mOhm, 7443552280	603.361.4457
5	C1, C2	2	Murata	1210	22uF Ceramic X5R 25V	978-779-3111
6	C5	1	Murata	1210	100uF Ceramic X5R 6.3V	978-779-3111
7	C4	1	Murata	0603	0.1uF Ceramic X7R 50V	978-779-3111
8	CBST	1	Murata	0603	22nF Ceramic X7R 50V	978-779-3111
9	CVCC	1	Murata	0603	4.7uF Ceramic X5R 10V	800-388-2496
10	CF1	1	Murata	0603	100pF Ceramic C0G 50V	978-779-3111
11	Cs2	1	Murata	0603	2.2nF Ceramic C0G 50V	978-779-3111
12	CSS1	1	Murata	0603	47nF Ceramic X7R 50V	978-779-3111
13	CP1	1	Murata	0603	100pF Ceramic C0G 50V	978-779-3111
14	CZ2	1	Murata	0603	8200pF Ceramic C0G 50V	978-779-3111
15	CZ3	1	Murata	0603	1500pF Ceramic C0G 50V	978-779-3111
16	R1	1	Panasonic	0603	10K Ohm Thick Film Res 1%	800-344-4539
17	R2	1	Panasonic	0603	1.91K Ohm Thick Film Res 1%	800-344-4539
18	R11	1	Panasonic	0603	0 Ohm Thick Film Res 1%	800-344-4539
19	RBST	1	Panasonic	0603	0 Ohm Thick Film Res 1%	800-344-4539
20	Rs2	1	Panasonic	0603	1 Ohm Thick Film Res 1%	800-344-4539
21	RZ2	1	Panasonic	0603	3.4K Ohm Thick Film Res 1%	800-344-4539
22	RZ3	1	Panasonic	0603	365 Ohm Thick Film Res 1%	800-344-4539
23	VIN, VOUT, GND, GND	4	Vector Electronic	.042 Dia	Test Point Post	800-344-4539

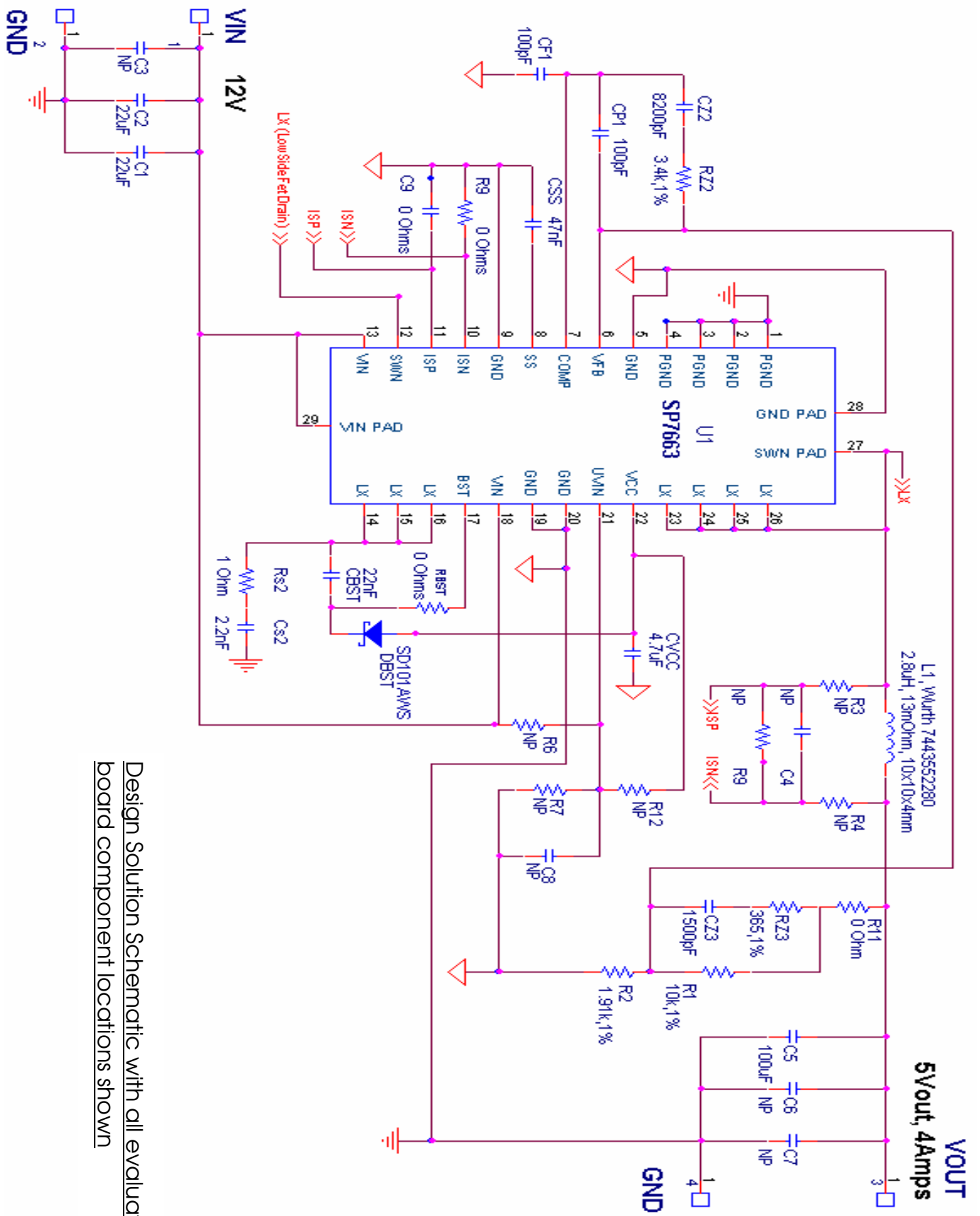

Design Solution Schematic with all evaluation board component locations shown

For further assistance:

Email: Sipexsupport@sipex.com
WWW Support page: <http://www.sipex.com/content.aspx?p=support>
Live Technical Chat: <http://www.geolink-group.com/sipex/>
Sipex Application Notes: <http://www.sipex.com/applicationNotes.aspx>



Sipex Corporation

Headquarters and
Sales Office
233 South Hillview Drive
Milpitas, CA95035
tel: (408) 934-7500
faX: (408) 935-7600

Sipex Corporation reserves the right to make changes to any products described herein. Sipex does not assume any liability arising out of the application or use of any product or circuit described herein; neither does it convey any license under its patent rights nor the rights of others.