

SP6136 Boost Regulator: 12V Input to 18V @ 0-2A Output

Designed by: Shahin Maloyan

Part Number: SP6136ER1

Application Description: High-voltage Point-of-Load


Electrical Requirements:

Input Voltage	12V
Output Voltage	18V
Output Current	0-2A

Circuit Description:

In this circuit SP6136 is configured as a boost converter to provide 18V output at 2A for Point-of-Load applications. The SP6136 is a high performance controller that provides the necessary functions required by a boost regulator: power-good output, adjustable UVLO and Enable input. High switching frequency (600kHz) minimizes solution cost and size.

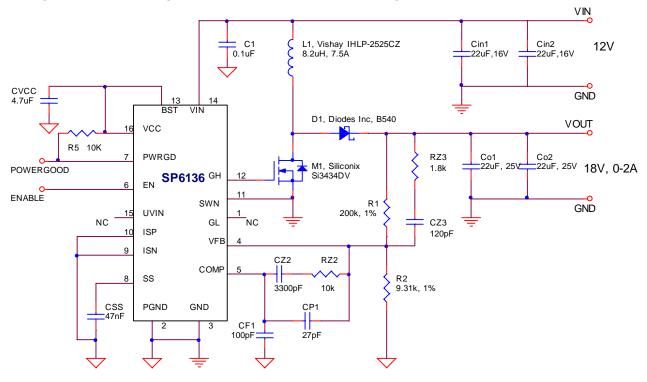This report includes the application schematic complete with component part numbers and figures 1-7 illustrating electrical performance of the design.



Circuit Schematic

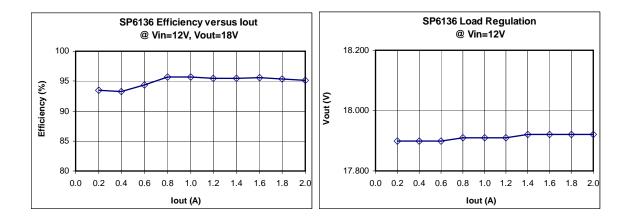


Figure 1: Efficiency Graph

Figure 2: VOUT Regulation Graph

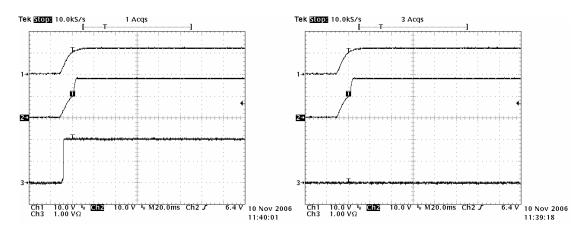


Figure 3. Startup at Io=2A, ch1:Vin, Ch2: Vout, ch3: Iout

Figure 4. Startup at Io=0A, ch1:Vin, Ch2: Vout, ch3: lout

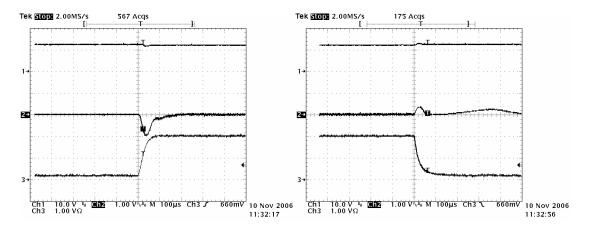


Figure 5. Step load 0.2-2A, ch1:Vin, Ch2: Vout, ch3: lout

Figure 6. Step load 2-0.2A, ch1:Vin, Ch2: Vout, ch3: lout


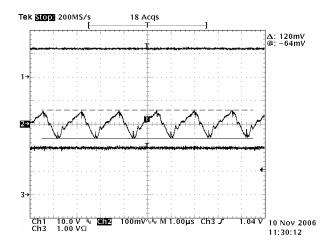


Figure 7. Output ripple is 120mV

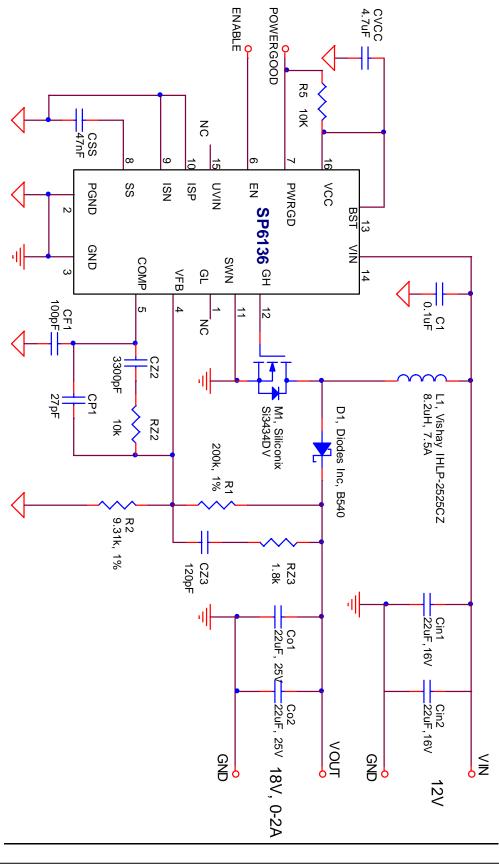

For further assistance:

Email: WWW Support page: Live Technical Chat: Sipex Application Notes:

Sipexsupport@sipex.com http://www.sipex.com/content.aspx?p=support http://www.geolink-group.com/sipex/ http://www.sipex.com/applicationNotes.aspx

