## **APPLICATION NOTE ANI10**



## Charge Pump Capacitor Selection Guide for 3V RS-232 Products

## Introduction

This Application note provides instructions for selecting the proper Charge Pump capacitor values (C1 - C4) for a given input voltage. This Application note applies to all 3V RS-232 transceivers unless stated within their respective data sheet. Any type of capacitor can be used and can be polarized or nonpolarized. If polarized capacitors are to be used, refer to the respective data sheet for correct orientation. By selecting the proper charge pump capacitor values, the designer can be assured of error free communications by reducing the amount of ripple voltage present on the driver outputs. The following chart illustrates the proper capacitor value for a given input voltage. If the designer wishes to reduce the driver output ripple further, the selected charge pump capacitor value can be doubled, for example; increase  $0.1\mu$ F capacitors at 3.0V operation to  $0.22\mu$ F. Increasing the charge pump capacitors two fold can also lower the input current drain by approximately 1 to 2mA depending on device being used.

Minimum Required Charge Pump Capacitor Value	
Input Voltage V <sub>CC</sub>	Charge pump capacitor value for SP32XX
3.0V to 3.6V	C1 - C4 = 0.1µF
4.5V to 5.5V	C1 = 0.047, C2-C4 = 0.33µF

This application note applies to the following devices with part numbers having a suffix of "E", "EH", "EB" or "EU".

SP3203 SP3220 SP3222 SP3223 SP3232 SP3238 SP3239 SP3243 SP3249 For further assistance:

Email: WWW Support page: Live Technical Chat: Sipex Application Notes:

Sipexsupport@sipex.com http://www.sipex.com/content.aspx?p=support http://www.geolink-group.com/sipex/ http://www.sipex.com/applicationNotes.aspx



## Sipex Corporation Headquarters and Sales Office 233 South Hillview Drive Milpitas, CA95035 tel: (408) 934-7500 fax: (408) 935-7600

Sipex Corporation reserves the right to make changes to any products described herein. Sipex does not assume any liability arising out of the application or use of any product or circuit described herein; neither does it convey any license under its patent rights nor the rights of others.